

CSE 535 : Lecture 2

Language-based Hardware Description

Washington University
Fall 2003

<http://www.arl.wustl.edu/arl/projects/fpx/cse535/>

Copyright 2003, John W Lockwood
Lockwood@arl.wustl.edu

Describing Hardware

- Schematic-based
 - Can be cumbersome for large projects
 - Requires version control to maintain libraries
- Language-based
 - Must express parallelism
 - C does not have explicit commands for parallelism
 - Must allow for *fine grain* parallelism
 - Allow *gate-level* parallelism where possible
 - Must be exact
 - Eliminate ambiguity
 - Synthesizable
 - Generate hardware from description

VHDL

- VHSIC Hardware Description Language
 - VHSIC = Very High Speed Integrated Circuit
 - IEEE 1076-1987
 - First ratified version of VHDL
 - Originally developed to *describe* digital system
 - [not build them!]
 - IEEE 1076-1993
 - Updated version, as used in textbook
 - IEEE 1164
 - Package for Synthesis

Example Entity declaration

```
ENTITY black_box IS PORT (  
    clk: IN  std_logic;  
    rst: IN  std_logic;  
    d:   IN  std_logic_vector(7 DOWNTO 0);  
    q:   OUT std_logic_vector(7 DOWNTO 0);  
    co:  OUT std_logic);  
END black_box;
```



The Architecture

- Architectures describe what is in the black box (i.e., the structure or behavior of entities)
- Descriptions can be either a combination of
 - Structural descriptions
 - Instantiations (placements of logic-much like in a schematic-and their connections) of building blocks referred to as components
 - Behavioral/Dataflow descriptions
 - Algorithmic (or “high-level”) descriptions:
 - IF a = b THEN state <= state5;
 - Boolean equations (also referred to as dataflow):
 - x <= (a OR b) AND c;

The Architecture Declaration

```
ARCHITECTURE arch_name OF entity_name IS
    -- optional signal declarations, etc.
BEGIN
    --VHDL statements
END arch_name;
```

- arch_name is an arbitrary name
- optional signal declarations are used for signals local to the architecture body (that is, not the entity's I/O).
- entity_name is the entity name
- statements describe the function or contents of the entity

Architecture Body Styles : Behavioral

```
ENTITY compare IS PORT (  
    a, b : IN std_logic_vector(0 TO 3);  
    equals: OUT std_logic);  
END compare;  
ARCHITECTURE behavior OF compare IS  
BEGIN  
    comp: PROCESS (a,b)  
    BEGIN  
        IF a = b THEN  
            equals <= '1' ;  
        ELSE  
            equals <= '0' ;  
        END IF ;  
    END PROCESS comp;  
END behavior;
```


Architecture Body Styles : Structural

```
ENTITY compare IS PORT (  
    a, b: IN std_logic_vector(0 TO 3);  
    equals: OUT std_logic);  
END compare;  
USE WORK.Gate-Library.ALL ;  
ARCHITECTURE structure OF compare IS  
    SIGNAL x : std_logic_vector (0 to 3) ;  
BEGIN  
    u0: xnor2 PORT MAP (a(0),b(0),x(0)) ;  
    u1: xnor2 PORT MAP (a(1),b(1),x(1)) ;  
    u2: xnor2 PORT MAP (a(2),b(2),x(2)) ;  
    u3: xnor2 PORT MAP (a(3),b(3),x(3)) ;  
    u4: and4 PORT MAP (x(0),x(1),x(2),x(3),equals) ;  
END structure;
```

Mixing Architecture Styles

- The various styles may be mixed in one architecture.
 
```
ENTITY logic IS PORT (  
    a,b,c: IN std_logic;  
    f: OUT std_logic);  
END logic;  
  
USE WORK.GateLibrary.ALL;  
ARCHITECTURE archlogic OF logic IS  
    SIGNAL d: std_logic;  
BEGIN  
    d <= a AND b; -- Behavioral  
    g1: nor2 PORT MAP (c, d, f); -- Structural  
END archlogic;
```



Native Operators

- Logical
 - AND, NAND
 - OR, NOR
 - XOR, XNOR
 - NOT
- Relational
 - = (equal to)
 - /= (not equal to)
 - < (less than)
 - <= (less than or equal to)
 - > (greater than)
 - >= (greater than or equal to)

VHDL Statements

- There are two types of statements
 - Sequential
 - Though hardware is concurrent, it may be modeled with algorithms, by a series of sequential statements
 - By definition, sequential statements are grouped using a process statement.
 - Concurrent
 - Statements outside of a process are evaluated concurrently during simulation
 - Processes are concurrent statements

Concurrent Statements

- Concurrent statements include:
 - Boolean equations
 - Conditional/selective assignments
 - Instantiations
- ```
-- Examples of boolean equations
x <= (a AND (NOT sel1)) OR (b AND sel1);
g <= NOT (y AND sel2);

-- Examples of conditional assignments
y <= d WHEN (sel1 = '1') ELSE c;
h <= '0' WHEN (x = '1' AND sel2 = '0') ELSE '1';

-- Examples of instantiation
inst: nand2 PORT MAP (h, g, f);
```

## The Process Statement

- An architecture can contain multiple processes.
- Each process is executed concurrently
- Statements within a process are sequential statements-they execute sequentially during simulation
- The statements with in a process not be sequential after synthesis

## The Process (cont)

```
label: PROCESS (sensitivity list)
-- variable declarations
BEGIN
-- sequential statements
END PROCESS label ;
```

- The process label and variable declarations are optional
- The process executes when one of the signals in the sensitivity list has an event (changes value).

## Process (cont)

- Processes are executing or suspended (active or inactive/awake or asleep)
- A process typically has a sensitivity list
  - When a signal in the sensitivity list changes value, the process is executed by the simulator
  - e.g., a process with a clock signal in its sensitivity list becomes active on changes of the clock signal
- All signal assignments occur at the **END PROCESS** statement in terms of simulation
  - The process is then suspended until there is an event (change in value) on a signal in the sensitivity list

## Selective Signal Assignment: select

- Assignment based on a selection signal
- **WHEN** clauses must be mutually exclusive
- Use a **WHEN OTHERS** to avoid latches
- Only one reference to the signal, only one assignment operator (**<=**)

```
WITH selection_signal SELECT
signal_name <= value_1 WHEN value_1,
 value_2 WHEN value_2,
 ...
 value_n WHEN value_n,
 value_x WHEN OTHERS;
```



## Combinational Logic with select

- The same 4-1 multiplexer is shown below

```
WITH s SELECT
 x <= a when "00" ,
 b when "01" ,
 c when "10" ,
 d when others ;
```

## Conditional Signal Assignment: when-else

- Signal is assigned a value based on conditions
- Any simple expression can be a condition
- Priority goes in order of appearance
- Only one reference to the signal, only one assignment operator (<=)
- Use a final ELSE to avoid latches

```
signal_name <= value_1 WHEN condition1 ELSE
 value_2 WHEN condition2 ELSE
 ...
 value_n WHEN conditionN ELSE
 value_x ;
```

## Combinational Logic (cont)

The same 4-1 multiplexer is shown below

```
x <= a when (s = "00") else
 b when (s = "01") else
 c when (s = "10") else
 d ;
```

## Combinational Logic (cont)

- The when conditions do not have to be mutually exclusive (as in with-select-when)
- A priority encoder is shown below

```
j <= w when (a = '1') else
 x when (b = '1') else
 y when (c = '1') else
 z when (d = '1') else
 '0' ;
```

## Sequential Statements: if-then-else

- Used to select a set of statements to be executed
- Selection based on a boolean evaluation of a condition or set of conditions

```
IF condition(s) THEN
 do something;
ELSIF condition_2 THEN -- optional
 do something different;
ELSE -- optional
 do something completely different;
END IF ;
```

## Avoiding the latch within an if-then-else

- Absence of ELSE results in implicit memory
- 4-1 mux shown below

```
mux4_1: process (a, b, c, d, s)
 begin
 if s = "00" then x <= a ;
 elsif s = "01" then x <= b ;
 elsif s = "10" then x <= c ;
 else x <= d ;
 end if;
 end process mux4_1 ;
```

## Sequential Statements: Case-When


```
CASE selection_signal
 WHEN value_1_of_selection_signal =>
 (do something) -- set of statements 1
 WHEN value_2_of_selection_signal =>
 (do something) -- set of statements 2
 ...
 WHEN value_N_of_selection_signal =>
 (do something) -- set of statements N
 WHEN OTHERS =>
 (do something) -- default action
END CASE ;
```

## The CASE Statement: 4-1 Mux


```
ARCHITECTURE archdesign OF design IS
 SIGNAL s: std_logic_vector(0 TO 1);
BEGIN
 mux4_1: PROCESS (a,b,c,d,s)
 BEGIN
 CASE s IS
 WHEN "00" => x <= a;
 WHEN "01" => x <= b;
 WHEN "10" => x <= c;
 WHEN OTHERS => x <= d;
 END CASE;
 END PROCESS mux4_1;
END archdesign;
```
 
## Synchronous Storage Elements

- Values change at times governed by clock




- Clock
  - Input to circuit

 

- Clock Event
  - Example: Rising edge

 
- Flip/Flop
  - Transfers Value From  $D_{in}$  to  $D_{out}$  on Clock event


 
## Edge Triggered Flop

```
entity flop is
 port (clk : in std_logic;
 Din : in std_logic;
 Dout : out std_logic);
end flop;
```

```
architecture behavioral of flop is
begin
 flop:process(clk)
 begin
 if (clk='1' and clk'event) then
 Dout <= Din;
 end if;
 end process flop;
end behavioral;
```



## Components

```
architecture structural of my_module is

 component flop32
 port (clk : in std_logic;
 Din : in std_logic_vector(31 downto 0);
 Dout : out std_logic_vector(31 downto 0));
 end component;

 ... other components ...

 DataReg: flop32
 port map (clk => clk,
 Din => d_mod_in,
 Dout => d_mod_out);

 ... other connections ...

end structural;
```

## Finite State Machine (FSM)

- Terminology
  - Time:  $t$
  - State:  $S$ 
    - State variables:  $S = \{ S_1, S_2 \dots S_k \}$
    - Current state:  $S(t)$
    - Next state:  $S(t+1)$
  - State transition function  $\delta()$ 
    - Assigns next state
- State Transition
  - $S(t+1) = \delta( X, S(t) )$

## State Declaration

```
type states is (init, pad, dout);
```



```
signal state, next_state : states;
```


## State Declaration

- Binary Encoding



- Number of Flops = 2

- One-Hot Encoding

 


- Number of Flops = 3

## State Encoding

- Given state machine with  $K$  states
- Choose encoding to maintain state
  - Binary Encoding
    - Number of Flops:  $O(\log_2 k)$
    - Minimizes number of Flops
  - One-Hot Encoding
    - Number of Flops:  $O(k)$
    - Reduces the next-state logic
    - Uses fewer levels of logic cells
    - Enables high-speed state machines
  - Automatic Encoding
    - Feature of many synthesis tools


## Implementation of the FSM

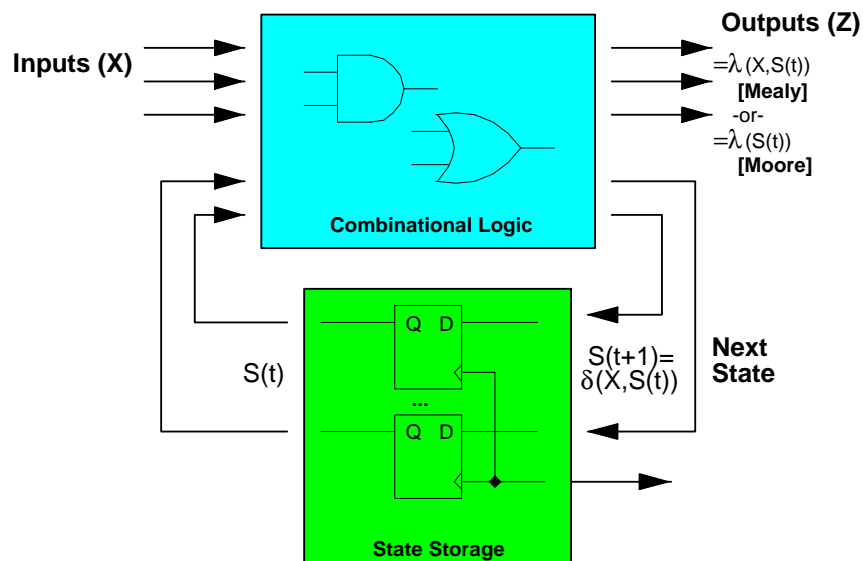


 
## State Transition

```
state_trans:process(state, soc_in, cntr, data_in)
begin
 case state is
 when init =>
 if (soc_in='1') then
 if (data_in(19 downto 4)=x"0005") then
 nxt_state <= pad;
 else
 nxt_state <= dout;
 end if;
 else
 nxt_state <= init;
 end if;
 ...
 end case;
end process state_trans;
```




## State Assignment Transition


```
clkd: process(clk)
begin
 if (clk'event and clk='1') then
 if (reset='1') then
 state <= init;
 else
 state <= next_state;
 end if;
 end if;
end process clkd;
```
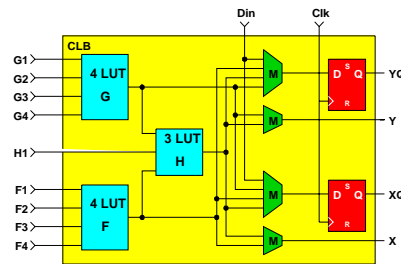
## Technology Mapping


- Map function into library of gates
- Timing optimization



## Reprogrammable Device Configuration

 


- CLB :
  - Primitive element of FPGA

 

- Routing Module :
  - Interconnection of Blocks

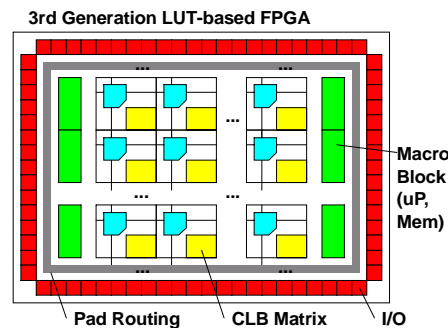- FPGA :
  - Matrix of CLBs and Routing Modules



## Final Design

- Physical Synthesis
  - Cell placement
  - Signal routing

