 


CS/EE 260 – Homework 5 Solutions


Spring 2000

- (MK 3-23) Construct a 10-to-1 line multiplexer with three 4-to-1 line multiplexers. The multiplexers should be interconnected and inputs labeled so that the selection codes 0000 through 1001 can be directly applied to the multiplexer selections inputs without added logic.

10:1 mux




Implementation using 4:1 muxes.

 


2. (MK 3-27) Implement a binary full adder with a dual 4-to-1 line multiplexer and a single inverter.

AB	C_i	S	C_o
00	0	0	0
00	1	1	0
01	0	1	0
01	1	0	1
10	0	1	0
10	1	0	1
11	0	0	1
11	1	1	1

 

 3. (MK 3-34) Design a combinational circuit that forms the 2-bit binary sum S_1S_0 of two 2-bit numbers A_1A_0 and B_1B_0 and has both input C_0 and a carry output C_2 . Do not use half adders or full adders, but instead use a two-level circuit plus inverters for the input variables, as needed. Design the circuit by starting with the following equations for each of the two bits of the adder.



$$S_0 = A_0 B_0 C_0 + A_0 B_0' C_0' + A_0' B_0 C_0' + A_0' B_0' C_0 = \text{odd}(A_0, B_0, C_0)$$

$$C_1 = A_0 B_0 + A_0 C_0 + B_0 C_0 = \text{majority}(A_0, B_0, C_0)$$

$$S_1 = \text{odd}(A_1, B_1, C_1) = \text{odd}(A_1, B_1, \text{majority}(A_0, B_0, C_0))$$

$$= A_1 B_1 \text{majority}(A_0, B_0, C_0) + A_1 B_1' \text{majority}(A_0, B_0, C_0)' \\ + A_1' B_1 \text{majority}(A_0, B_0, C_0)' + A_1' B_1' \text{majority}(A_0, B_0, C_0)$$

$$= (A_1 B_1 + A_1' B_1') \text{majority}(A_0, B_0, C_0) + (A_1 B_1' + A_1' B_1) \text{majority}(A_0, B_0, C_0)'$$


$$= (A_1 B_1 + A_1' B_1') (A_0 B_0 + A_0 C_0 + B_0 C_0) + (A_1 B_1' + A_1' B_1) (A_0' B_0' + A_0' C_0' + B_0' C_0')$$

$$= A_1 B_1 A_0 B_0 + A_1 B_1 A_0 C_0 + A_1 B_1 B_0 C_0 + A_1' B_1' A_0 B_0 + A_1' B_1' A_0 C_0 + A_1' B_1' B_0 C_0 \\ + A_1' B_1 A_0' B_0' + A_1' B_1 A_0' C_0' + A_1' B_1 B_0' C_0' + A_1 B_1' A_0' B_0' + A_1 B_1' A_0' C_0' + A_1 B_1' B_0' C_0'$$

$$C_2 = \text{majority}(A_1, B_1, C_1) = \text{majority}(A_1, B_1, \text{majority}(A_0, B_0, C_0))$$

$$= A_1 B_1 + A_1 \text{majority}(A_0, B_0, C_0) + B_1 \text{majority}(A_0, B_0, C_0)$$
 
$$= A_1 B_1 + A_1 (A_0 B_0 + A_0 C_0 + B_0 C_0) + B_1 (A_0 B_0 + A_0 C_0 + B_0 C_0)$$



4. This problem is to design a simple 4 bit arithmetic unit. Your circuit will have two data inputs $A=a_3a_2a_1a_0$ and $B=b_3b_2b_1b_0$ and a data output $X=x_3x_2x_1x_0$. It will also have a control input $C=c_2c_1c_0$ which determines what operation your circuit will perform.

if $C=0$ then the output X is equal to input A

if $C=1$ then the output X is equal to input B

if $C=2$ then the output X is equal to the 2's complement of input A

if $C=3$ then the output X is equal to the 2's complement of input B

if $C=4$ then the output X is equal to $A+B$ where A and B are interpreted as unsigned integer values in the range 0..15

if $C=5$ then the output X is equal to $A+B$ where A and B are interpreted as signed integer values in the range -8..+7 (2s complement)

if $C=6$ then the output X is equal to $A-B$ where A and B are interpreted as signed integer values in the range -8..+7 (2s complement)

if $C=7$ then the output X is equal to $B-A$ where A and B are interpreted as signed integer values in the range -8..+7 (2s complement)

In addition, your circuit will have a status output V which is 1, if the requested operation results in an invalid result. For example, negating an input whose value is -8 should cause the V output to go high. An unsigned addition of values 8 and 13 should also cause the V bit to go high.

As a first step in designing your circuit, draw a *block diagram* that includes a 4 bit adder, one or more 1's complement circuits, incrementers and multiplexors. Include a control block that the *C* input connects to and that generates the *V* output and the control signals for the other components. Show each circuit component as a block labeled by its function (e.g. adder) and with all inputs and outputs clearly labeled.

Write logic equations for each output of the control block that will cause the circuit as a whole to implement the specification given above.

Complete your design using the schematic editor. Use only AND, OR, EXOR gates and inverters. On the printout of the schematic, outline in pencil the gates that correspond to the blocks in your block diagram and label them as in your block diagram. Arrange your schematic so that it corresponds as closely as possible to your block diagram.

Simulate your design for the following inputs and verify that the results are correct.

$C=0, A=5; C=1, B=10; C=2, A=6; C=3, B=-8; C=4, A=5, B=14; C=4, A=5, B=7; C=5, A=6, B=5; C=5, A=3, B=4; C=6, A=5, B=2; C=6, A=4, B=6; C=6, A=4, B=-6; C=6, A=2, B=3; C=7, A=5, B=-6; C=7, A=-2, B=6$

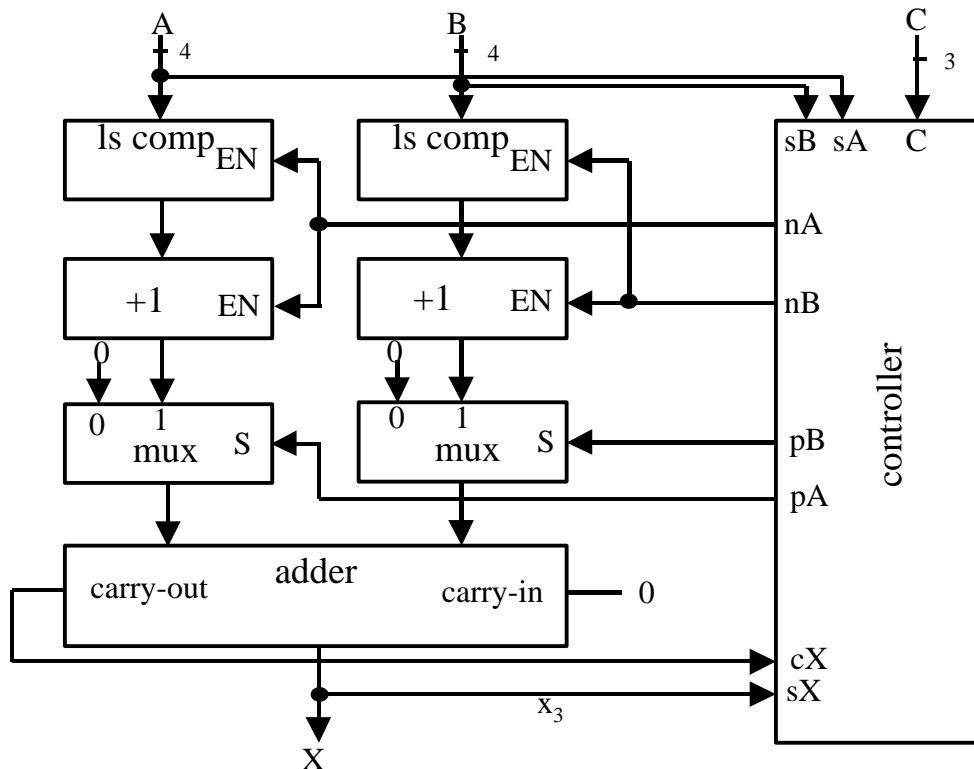


Table for control signals:

C	nA	pA	nB	pB	V
0	0	1	X	0	0
1	X	0	0	1	0
2	1	1	X	0	$sA \cdot sX$
3	X	0	1	1	$sB \cdot sX$
4	0	1	0	1	cX
5	0	1	0	1	$(sA=sB) \cdot (sA \neq sX)$
6	0	1	1	1	$(sA \neq sB) \cdot (sA \neq sX)$
7	1	1	0	1	$(sA \neq sB) \cdot (sB \neq sX)$



$$nA = (C=2) + (C=7)$$

$$pA = C_2 + C_0'$$


$$nB = (C=3) + (C=6)$$

$$pB = C_2 + C_0$$
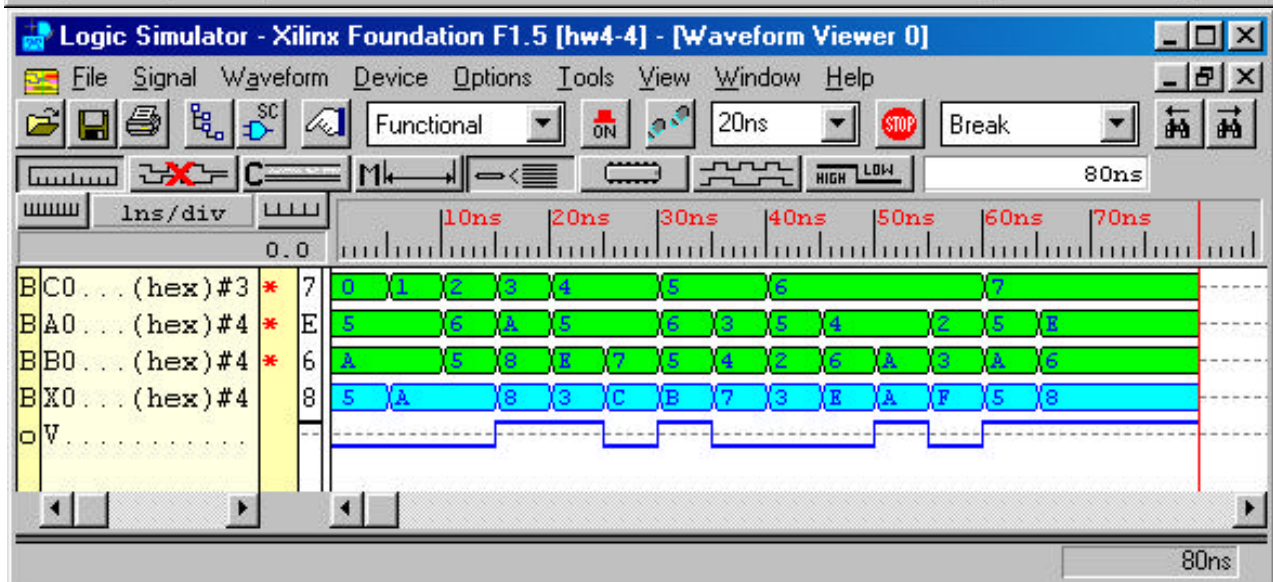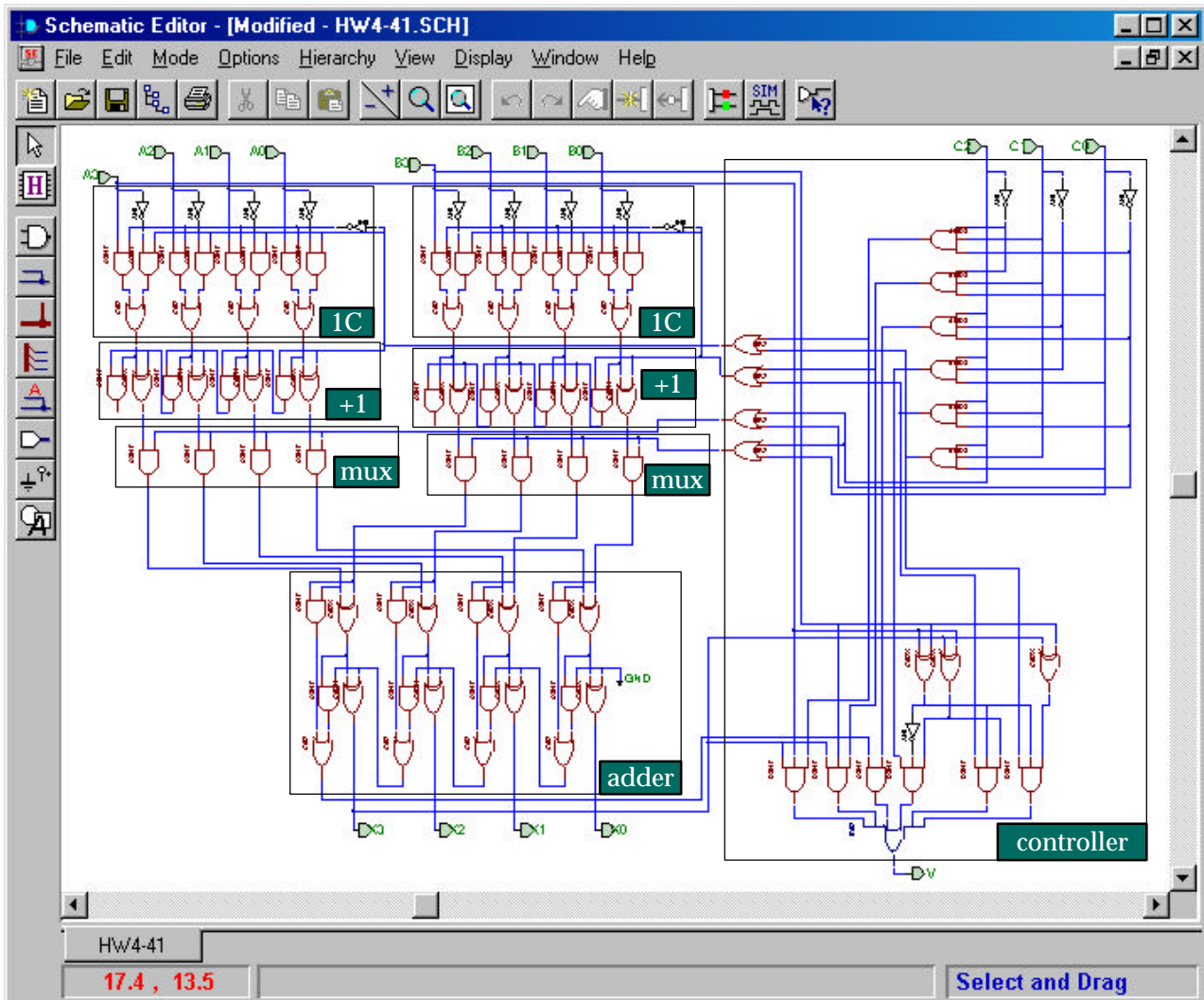
$$V = (C=2) \cdot sA \cdot sX + (C=3) \cdot sB \cdot sX + (C=4) \cdot cX + (C=5) \cdot (sA \oplus sB)' \cdot (sA \oplus sX) \\ + (C=6) \cdot (sA \oplus sB) \cdot (sA \oplus sX) + (C=7) \cdot (sA \oplus sB) \cdot (sB \oplus sX)$$



5. Draw (by hand) a schematic diagram for a 2 input, 4 output decoder using simple 2 input gates. Label each input, output and gate. Write a structural VHDL specification that directly implements the circuit in your schematic. Simulate your decoder on all possible inputs. Write a dataflow VHDL specification of the decoder and simulate this version as well. Hand in the schematic, the VHDL listings and the waveforms from your simulation runs.

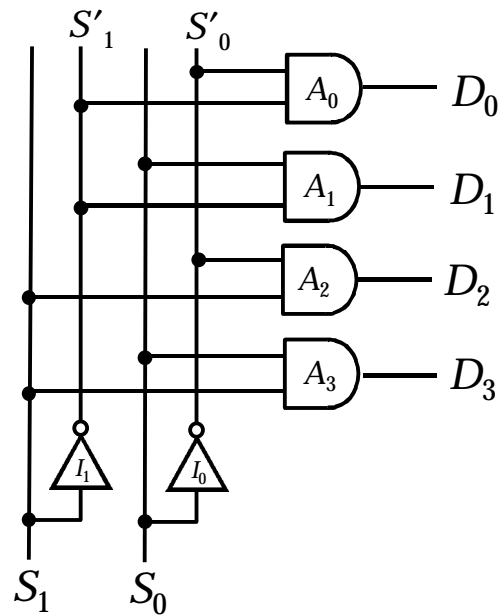

hw55a.vhd - HDL Editor

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity hw5_5 is
5      port (
6          s1, s0: in STD_LOGIC;
7          d0, d1, d2, d3: out STD_LOGIC
8      );
9  end hw5_5;
10
11 architecture hw5_5_arch of hw5_5 is
12
13 component INU
14     port(i: in STD_LOGIC; o: OUT STD_LOGIC);
15 end component;
16
17 component AND2
18     port(i0,i1: in STD_LOGIC; o: OUT STD_LOGIC);
19 end component;
20
21 signal s0b, s1b: STD_LOGIC;
22
23 begin
24     i0: INU port map(i => s0, o => s0b);
25     i1: INU port map(i => s1, o => s1b);
26     a0: AND2 port map(i0 => s1b, i1 => s0b, o => d0);
27     a1: AND2 port map(i0 => s1b, i1 => s0, o => d1);
28     a2: AND2 port map(i0 => s1, i1 => s0b, o => d2);
29     a3: AND2 port map(i0 => s1, i1 => s0, o => d3);
30 end hw5_5_arch;

```

For Help, press F1 Ln 28, Col 39 VHDL NUM

Logic Simulator - Xilinx Foundation F1.5 [hw55a]

File Signal Waveform Device Options Tools View Window Help

Functional ON 10ns STOP Break

Waveform Viewer 0

500ps/div 40ns

0.0 5ns 10ns 15ns 20ns 25ns 30ns 35ns

Signal	Direction	Initial Value
i S0	B0	0
i S1	B1	0
o D0		
o D1		
o D2		
o D3		

40ns

hw55b.vhd - HDL Editor

File Edit Search View Synthesis Project Tools Help

```

1 library IEEE;
2 use IEEE.std_logic_1164.all;
3
4 entity hw55b is
5     port (
6         s1, s0: in STD_LOGIC;
7         d0, d1, d2, d3: out STD_LOGIC
8     );
9 end hw55b;
10
11 architecture hw55b_arch of hw55b is
12 begin
13     d0 <= (not s1) and (not s0);
14     d1 <= (not s1) and (    s0);
15     d2 <= (    s1) and (not s0);
16     d3 <= (    s1) and (    s0);
17 end hw55b_arch;
18

```

For Help, press F1 Ln 16, Col 1 VHDL NUM

Logic Simulator - Xilinx Foundation F1.5 [hw55b]

File Signal Waveform Device Options Tools View Window Help

Functional ON 10ns STOP Break

Waveform Viewer 0

500ps/div 0.0 5ns 10ns 15ns 20ns 25ns 30ns 3

40ns

Time (ns)	iS1	iS0	oD0	oD1	oD2	oD3
0.0 - 5.0	0	0	1	0	0	0
5.0 - 10.0	0	1	0	1	0	0
10.0 - 15.0	1	0	0	0	1	0
15.0 - 20.0	1	1	0	0	0	1
20.0 - 25.0	0	0	1	0	0	0
25.0 - 30.0	0	1	0	1	0	0
30.0 - 35.0	1	0	0	0	1	0
35.0 - 40.0	1	1	0	0	0	1

